

# MrGoff.com Comp Sys Test (Offline)

Draw the logic gate symbol and state the Boolean expression that represents the NOR gate. (2 marks)

Logic gate	Logic statement

Show the truth table for a NAND gate. (2 marks)

Why are NAND gates referred to as universal gates? (1 mark)

---

---

Explain how the full adder works. (3 marks)

---

---

---

---

---

---

---

---

# MrGoff.com Comp Sys Test (Offline)

Explain how you could build a circuit to add N bits using full adders (2 marks)

---

---

Identify the inputs of a d-type flip-flop (2 marks)

---

---

Simplify the boolean expression  $A.B+A+B$  (2 marks)

---

---

---

---

---

---

Simplify the expression  $(A + B).(B.C)+(C.B)$  (2 marks)

---

---

---

---

---

---

---

---

# MrGoff.com Comp Sys Test (Offline)

Simplify the expression  $\overline{\overline{A + \overline{B \cdot A}}}$  (4 marks)

---

---

---

---

---

---

---

---

---

---

---

---